

ANALOG SYSTEMS : PROBLEM SET 6

Problem 1

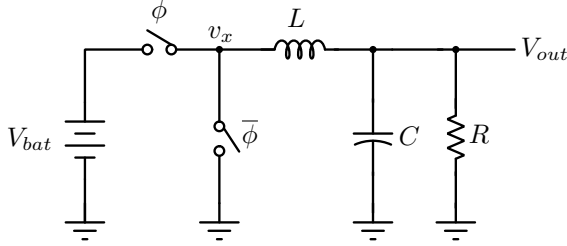


Figure 1: Circuit for Problem 1.

Fig. 1 shows a buck converter. The battery voltage V_{bat} is 5 V. ϕ and $\bar{\phi}$ are complementary switch drive signals. The duty cycle of ϕ is denoted by D . The switching frequency is 1.5 MHz. $L = 2.2 \mu\text{H}$ and $C = 22 \mu\text{F}$. The load resistor $R = 10 \Omega$.

- Determine D needed to achieve $\overline{V_{out}} = 3.3 \text{ V}$.
- Determine the transfer function from v_x to V_{out} .
- Using the observation that the pole frequency of the LC filter is much lower than the switching frequency, determine the ripple in the inductor current and output voltage.
- Sketch the current waveforms in the inductor and capacitor in steady state.
- Sketch the voltage waveform V_{out} in steady state.

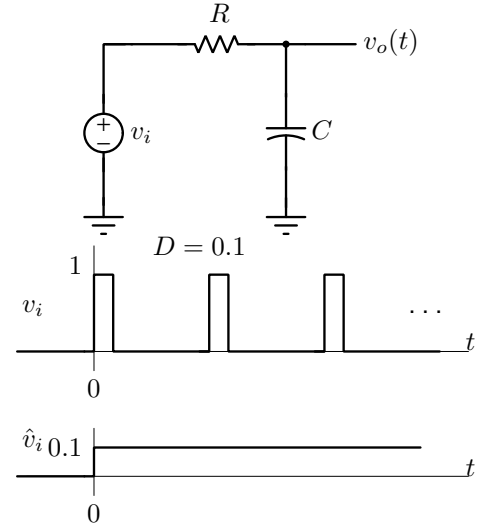


Figure 2: Circuit for Problem 2.

Problem 2

In class, we saw that the response of a “slow” linear time-invariant system to a rapidly varying input like v_i in Fig. 2 is approximately the same as that due to \hat{v}_i . In this problem, we will convince ourselves of this by working a specific example.

Assume that v_i has a frequency of 1 MHz, and a duty cycle of 10%. $RC = 1 \text{ ms}$. On the same graph, plot $v_o(t)$ when the input is $v_i(t)$, and when it is $\hat{v}_i(t)$.

Problem 3

As usual, the switching period T_s is much smaller than the time-constant of the LC network. S1 and S2 are controlled by complementary waveforms, and the waveform controlling S1 is shown in the figure. Determine the average output voltage v_o , and the average current drawn

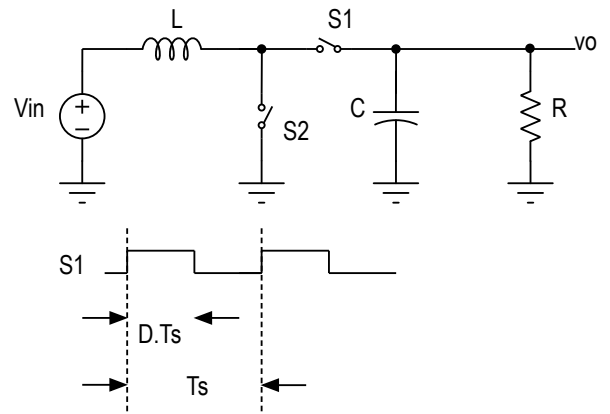


Figure 3: Circuit for Problem 3.

from the source. Draw the steady state current and voltage waveforms through/across the inductor and capacitor.